



KTU NOTES APP



www.ktunotes.in


POWER SUPPLIES

MODULE - II

POWER SUPPLIES

1. Regulated Power supply
2. Unregulated power supply.

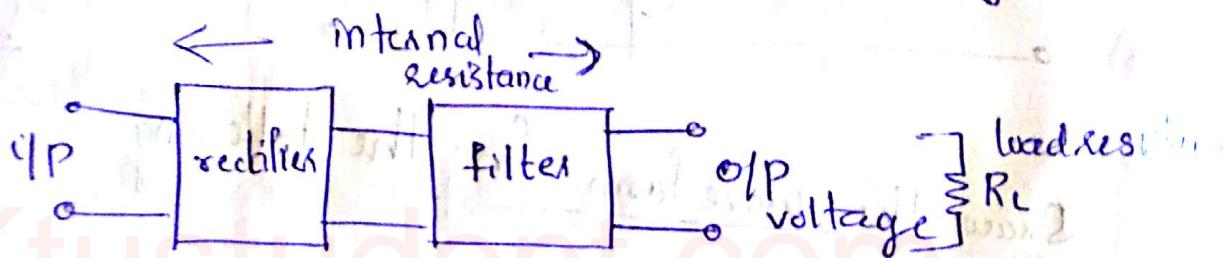D) Rectifier \rightarrow filter: unregulated power supply.



disadv


1) According to R_L varies, V_o also varies.

$$\begin{aligned} R_L \uparrow & V_o \uparrow \\ R_L \downarrow & V_o \downarrow \end{aligned}$$

2) Fluctuation in i/p signal varies the o/p signal.

3) Internal resistance

Regulated Power supply

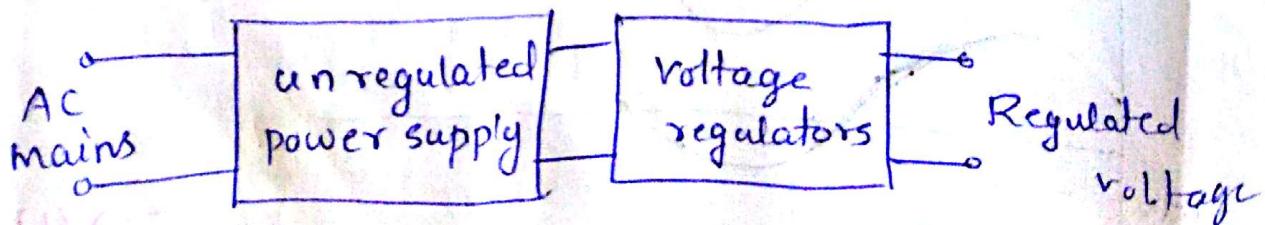


Voltage Multiplier

Voltage Doubler

- Half wave voltage doubler
- full wave voltage doubler

Half wave voltage doubler

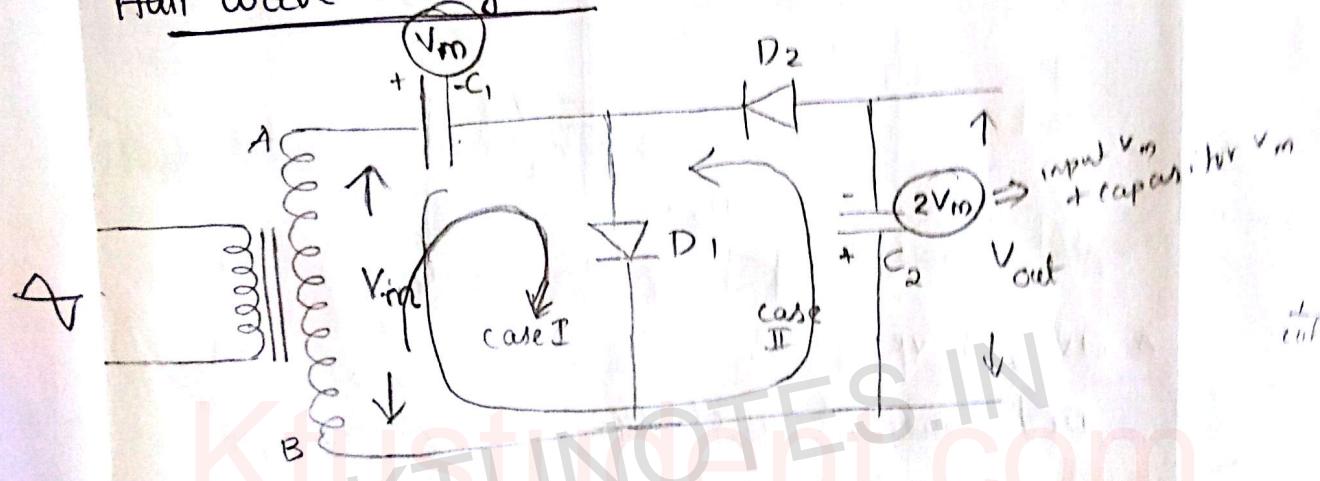

case I $A:+ve, B:-ve$

$D_1 \rightarrow$ forward biased
 $D_2 \rightarrow$ reverse, C_1 charges


case II $A:-ve, B:+ve$

$D_1 \rightarrow$ reverse

$D_2 \rightarrow$ forward, C_2 charges

(1)

Full wave voltage doubler

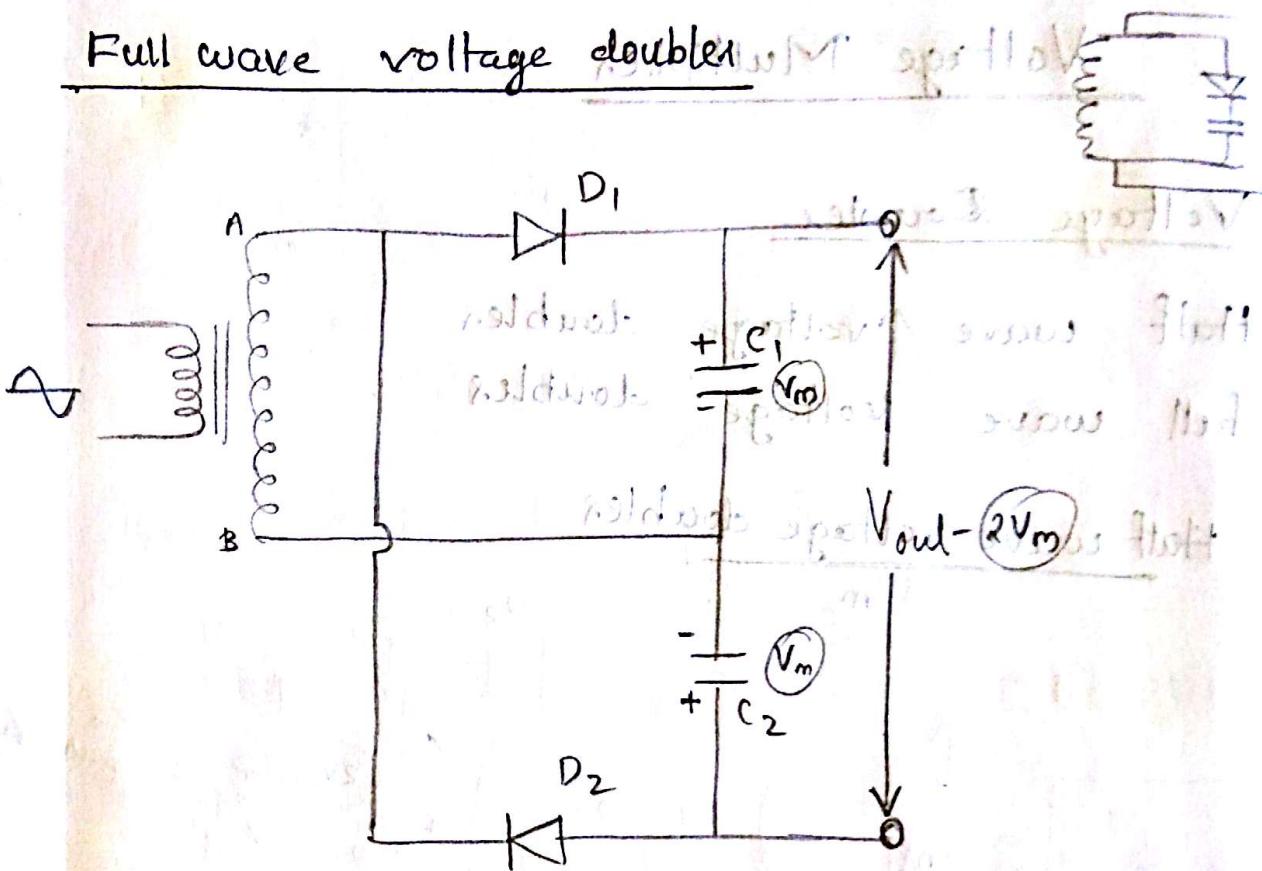

$A \rightarrow +ve, B - ve$


D_1 forward, C_1 charges

$A \rightarrow -ve, B + ve$

D_2 C_2 charges



V_{out} across L_1 & C_2 $\therefore V_{out} = V_m$

Voltage tripler circuit

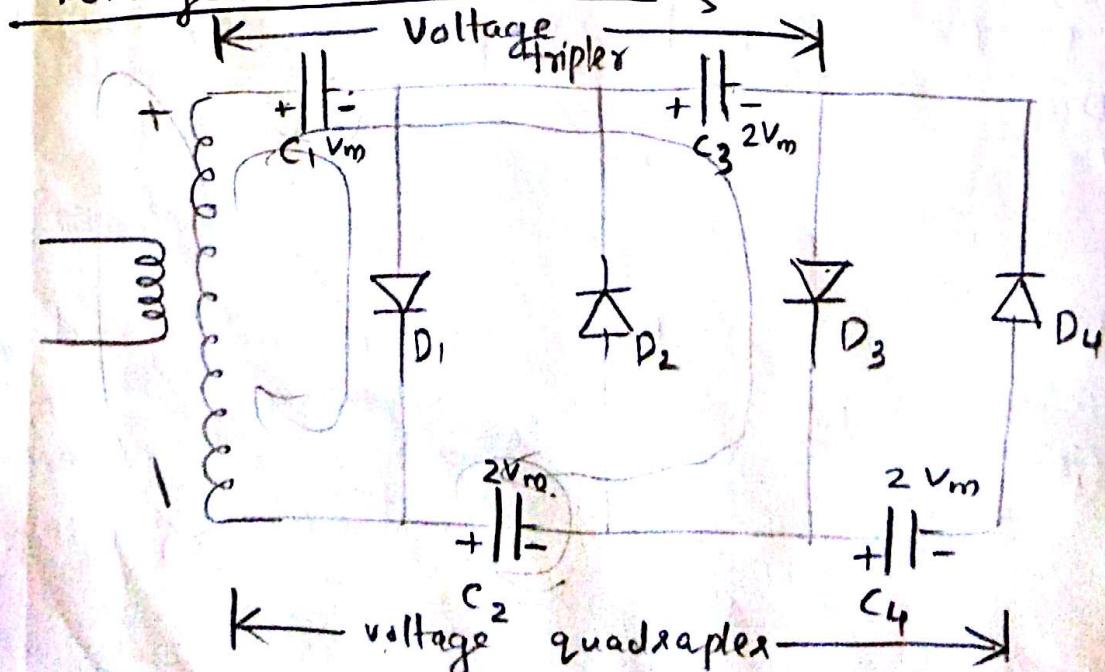


(2)

Sweep Circuit

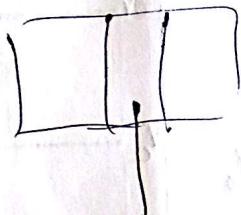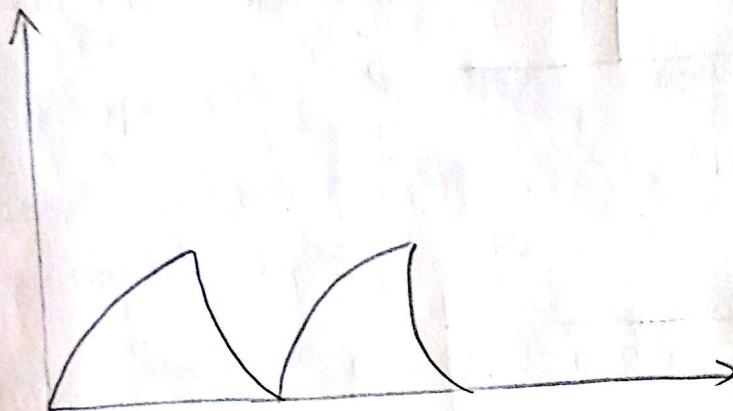

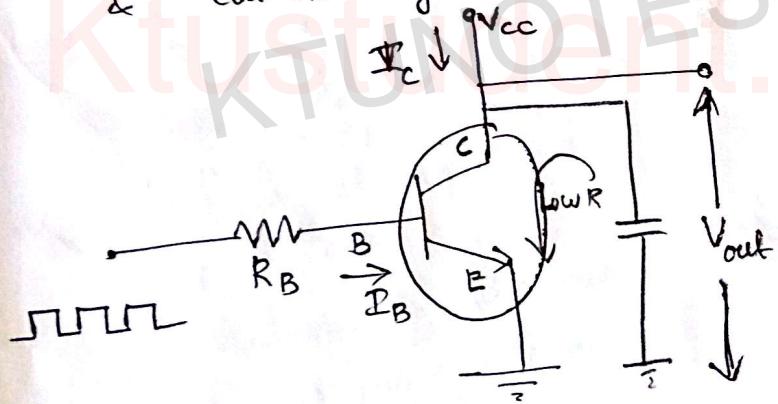Transistor works in saturation region & cut-off region in a sweep circuit



$$\frac{I_c}{I_B} = \beta$$

$$V_o = V_{cc} - I_c R_C$$


$$\text{when } I_B = 0, \quad I_c = \beta I_B = 0$$

$$\therefore V_o = V_{cc} - 0 \times R_C$$


$$\underline{\underline{V_o = V_{cc}}}$$

(3)

T_{Vi}

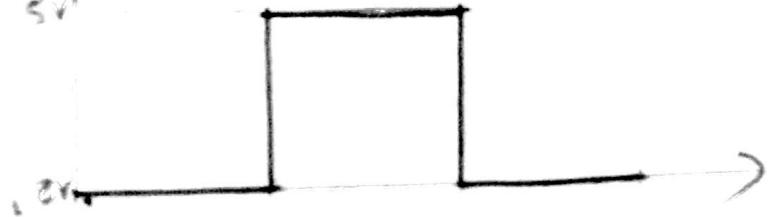

T_{V_o}

 

sweep waveform



(4)

Series voltage regulator

Shunt voltage regulator

Characteristics of voltage regulator

- 1) Load regulation (LR)
- 2) Minimum resistance $R_{L\min}$
- 3) Lin Regulation or source regulation (STR)
- 4) Output impedance
- 5) Ripple Rejection.

Load regulation (LR)

$$LR = V_{NL} - V_{FL}$$

V_{NL} - Voltage at no load
i.e., $R_L = \infty$

V_{FL} = Voltage at full load
i.e., R_L is minimum.

In ideal case $LR = \text{zero}$

Minimum Resistance ($R_{L\min}$)

It is the load resistance when load current is maximum.

$$R_{L(\min)} = \frac{V_{FL}}{I_{L(\max)}}$$

Line Regulation or Source Regulation

$$SR = V_{HL} - V_{LL}$$

V_{HL} = maximum source voltage

V_{LL} = minimum source voltage

$$SR\% = \frac{V_{HL} - V_{LL}}{V_{HL}}$$


Output impedance

Resistance offered by the circuit.

Ripple Rejection

ripples zero.

Zener Regulation

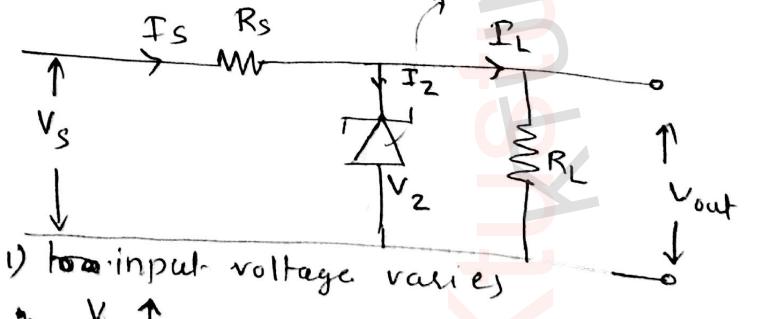

$$I_S = I_z + I_L \quad \text{constant}$$

$I_S \uparrow \quad I_z \uparrow \quad I_L \downarrow$

$V_{in} \downarrow \quad I_S$

V_z constant

$$V_z = I_z \cdot R$$

$$I_L R_L = \text{constant}$$

$\because I_L$ is constant

3) R_L varies

$R_L \uparrow$

$$I_s = I_z + I_L$$

$$R_s = \frac{V_s - V_z}{I_s}$$

Ques?


For the circuit shown $R_s = 20\Omega$, $V_z = 18V$
 $R_L = 200\Omega$. If V_{in} can vary from 20V

Find 1) The minimum & maximum current in zener diode

2) The min & max. power dissipated by diode

3) The maximum rated power dissipation that R_s should have.

$$\frac{V_s - V_z}{I_s}$$

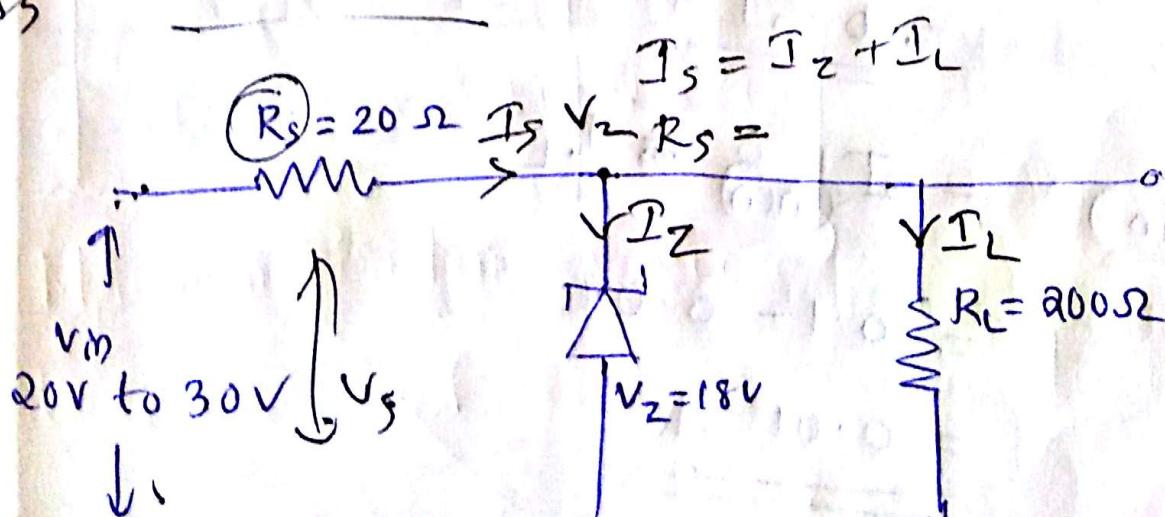

$$V_{in(min)} = 20 \text{ V}$$

$$R_S = 20 \Omega$$

$$V_Z = 18 \text{ V}$$

$$V_{in(max)} = 30 \text{ V}$$

$$R_L = 200 \Omega$$

$$I_{S(min)} = \frac{V_S - V_Z}{R_S} = \frac{20 - 18}{20} = \frac{2}{20} = 0.1 \text{ A}$$

$$I_{S(max)} = \frac{V_S - V_Z}{R_S} = \frac{30 - 18}{20} = \frac{12}{20} = \frac{6}{10} = 0.6 \text{ A}$$

$$I_S = I_Z + I_L \Rightarrow I_Z = I_S - I_L$$

$$V_{out} = V_Z$$

$$\therefore I_L = \frac{V_{out}}{R_L} = \frac{9}{200} = 0.045 \text{ A}$$
$$= 200 \times 0.045 = 0.09 \text{ A}$$

$$I_{Z(max)} = I_{S(max)} - I_L$$

$$= 0.6 - 0.09 = 0.51 \text{ A}$$

$$= \underline{\underline{0.51 \text{ A}}}$$

$$I_{Z(min)} = I_{S(min)} = I_L$$

$$= 0.1 - 0.09$$

$$= \underline{\underline{0.01 \text{ A}}}$$

b) Min power, $P_{min} = I_Z \cdot V_Z = 0.01 \times 18 = 0.18 \text{ W}$

Max power, $P_{max} = 0.51 \times 18 = 9.18 \text{ W}$


$$P_s = I^2 R = I_{sc(max)}^2 \cdot R_s$$

$$= 0.6^2 \times 20 = \underline{\underline{7.2 \text{ W}}}$$



$$FV = 0.6 \times 20 = 12$$

F8

Series Regulators

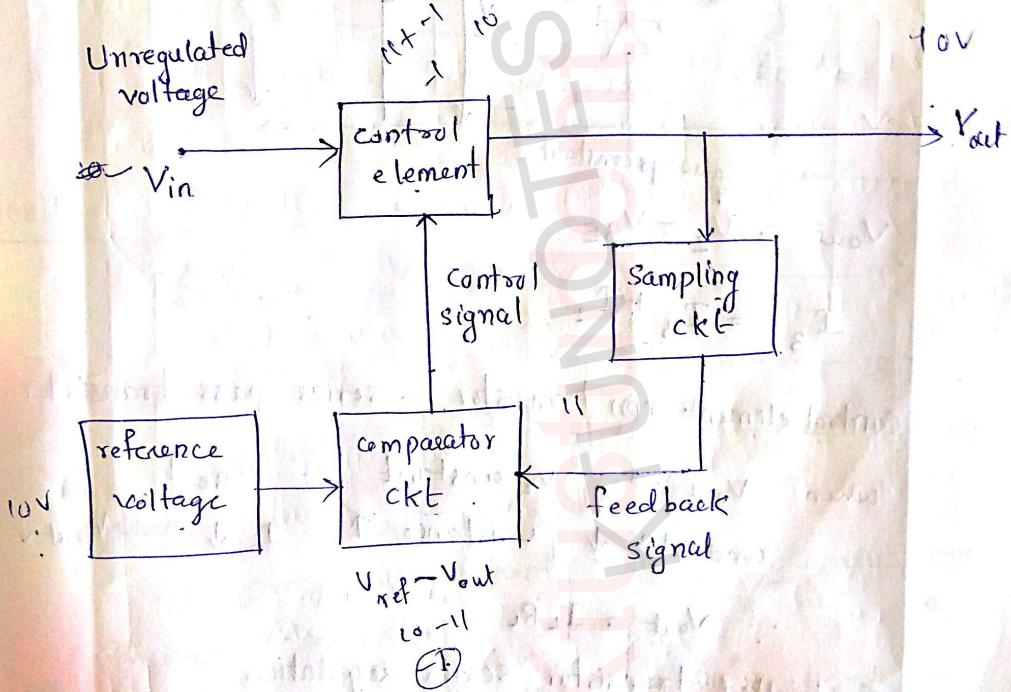

Transistor Series Regulation

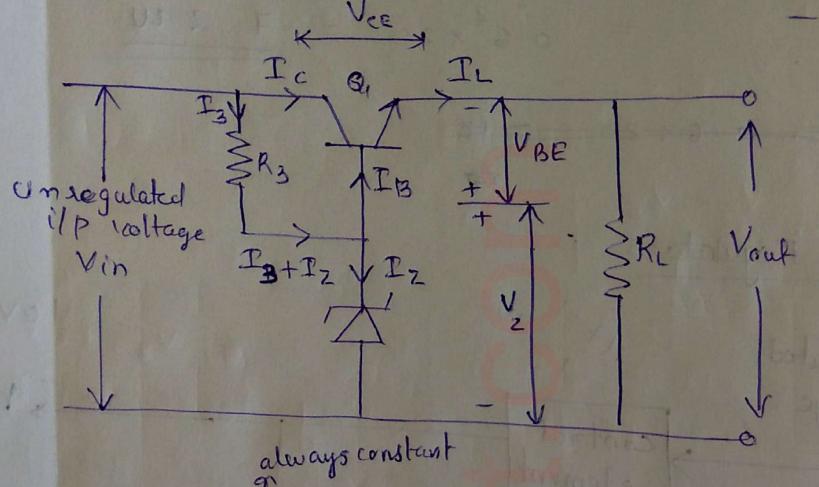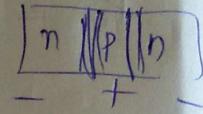

$$V_{out} = V_z - V_{BE}$$

$$I_3 = I_B + I_z$$


Control element npn transistor - series pass transistor

when $V_{out} \uparrow$ V_z constant $\therefore V_{BE} \downarrow$

\therefore conductance \downarrow resistance \uparrow $I_L \downarrow \therefore V_{out} \downarrow$

$$\therefore V_{out} = I_L R_L$$

Controlled transistor series regulation

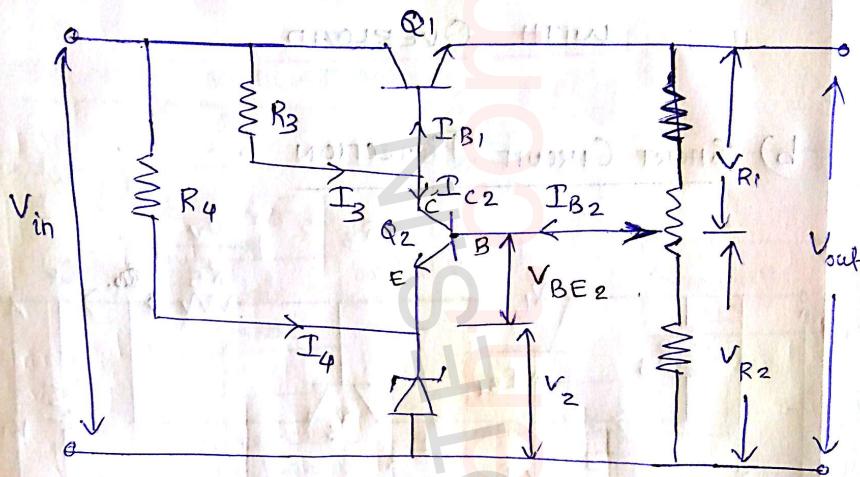

31/08/16

$$V_{R2} = V_{BE2} + V_z \quad (1)$$

$$V_{out} = V_{R1} + V_{R2} \quad (2)$$

$$I_3 = I_{B1} + I_{C2} \quad (3)$$

When $V_{out} \uparrow$, $V_{R2} \uparrow$
 since V_z constant $V_{BE2} \uparrow$, conduction

through transistor \uparrow $\therefore I_{C2} \uparrow$

since I_3 is almost constant

\therefore acc. Acc. (3) $I_{B1} \downarrow$


$\therefore V_{R1} \downarrow$

$\therefore V_{out}$ become constant.


CONTROLLED TRANSISTOR SERIES REGULATOR

WITH OVERLOAD

b) SHORT CIRCUIT PROTECTION

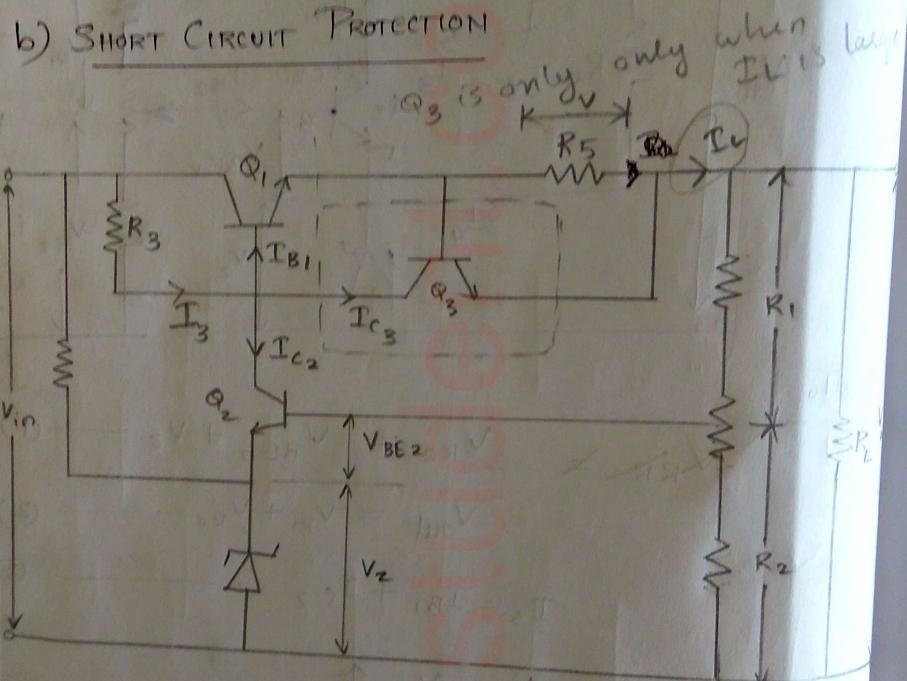


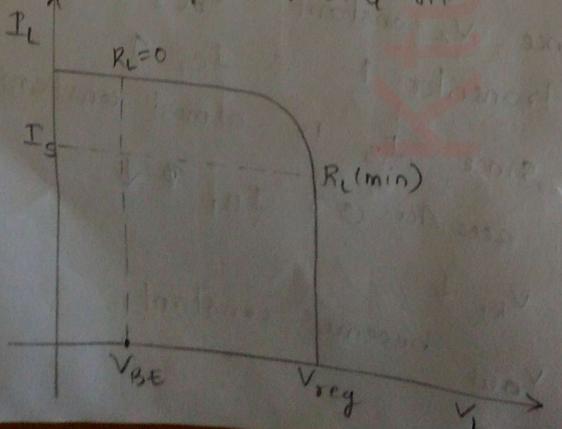at normal stage $V \downarrow \therefore Q_3 \text{ off}$




SHUNT

SHUNT REGULATION

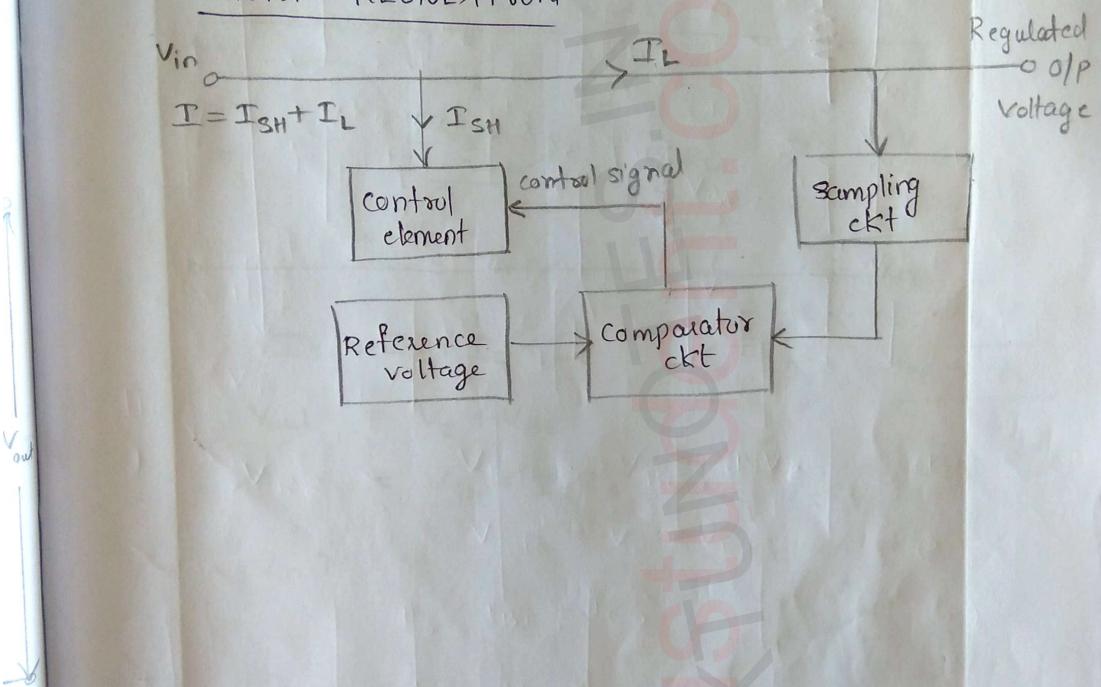

SHUNT REGULATION

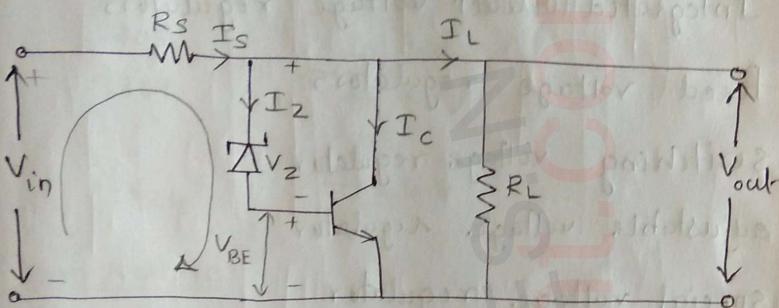

$$I_s = I_z + I_c + I_L$$

$$V_{out} = V_z + V_{BE}$$

$$= V_{in} - I_s R_s$$

$V_{in} \uparrow$

$$V_{in} - I_s R_s - V_z - V_{BE} = 0$$

$$(V_{in} - I_s R_s = V_z + V_{BE})$$

$V_{in} \uparrow$

$V_{in} - I_s R_s \uparrow$

$V_z \text{ constant}$

$V_{BE} \uparrow$

$V_{out} \uparrow$

when $V_{in} \downarrow$ follow below

$$V_{in} - I_s R_s \downarrow$$

$V_z \text{ constant}$

$V_{BE} \downarrow$

$V_{out} \downarrow$

IC Regulators


Integrated circuit voltage regulators

fixed voltage regulators

switching voltage regulator


adjustable voltage regulator

special voltage regulator

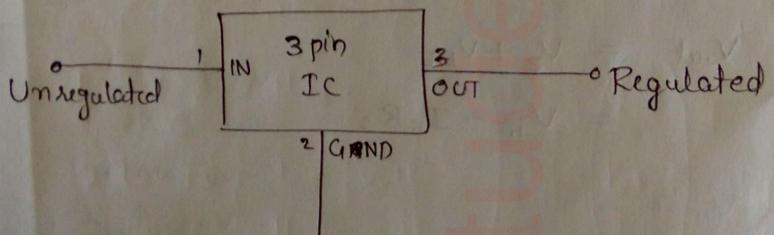

Coupling Capacitors

100 mA - 5A Fixed voltage regulator

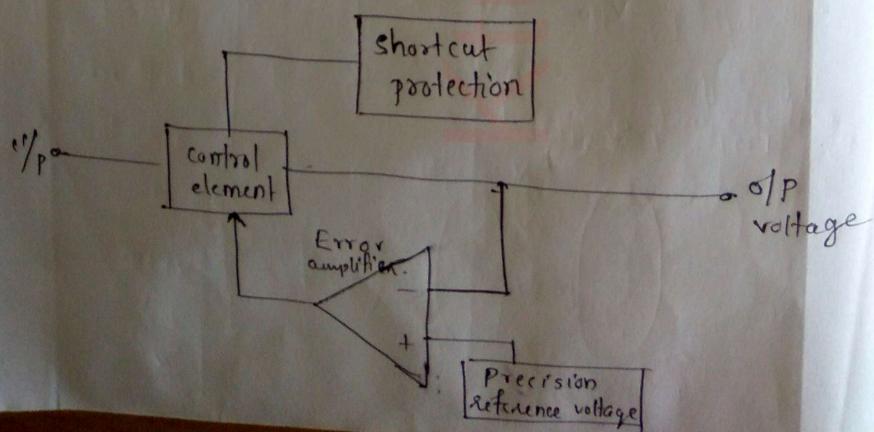

Positive Voltage regulators

IC 78XX series 5 to 24V.

7805 → 5V

7809 → 9V

7824 → 24V

Drop voltage

min. 2 volt

7805 min i/p v = 7V

max i/p v = 35V

Negative voltage regulators

IC 79XX series

7905 → -5V

!

7924 → -24V

7902 → -2V


7905.2 → -5.2V

Adjustable voltage regulator

1) Adjustment terminal

2) i/P

3) o/P

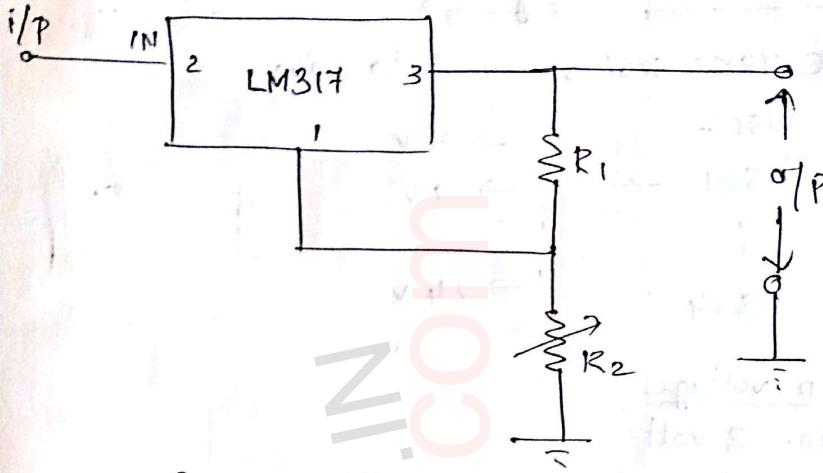

varies from 1.2 - 3.7

05/09/16


IC-723 voltage regulator

2V to 7V : low voltage regulator

>7V : High voltage regulator

14 pin IC

NC	1	14	NC
current limit	2	13	Frequency compensation
current sense	3	12	- V ⁺
INV	4	11	- V _C
V _{IN}	5	10	- V _{out}
V _{ref}	6	9	- V ₂
V ⁻	7	8	- NC

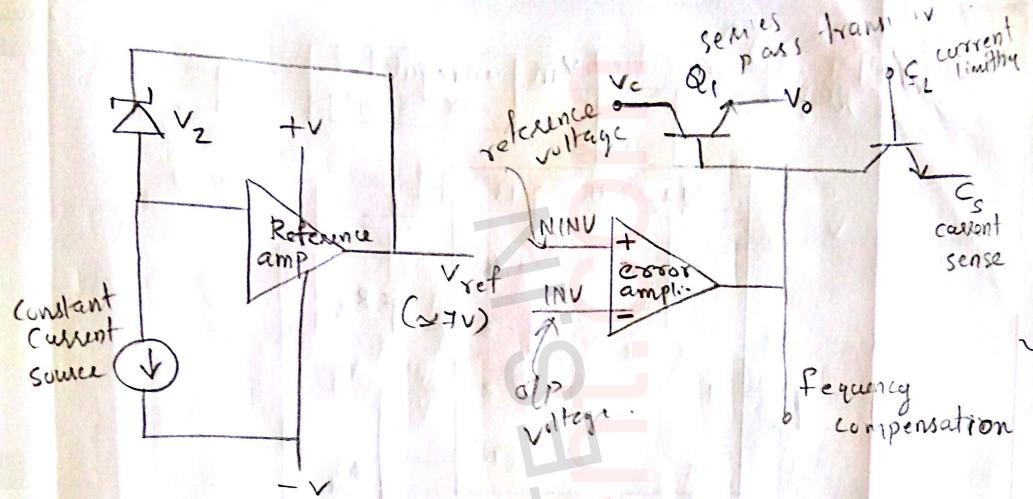

NC - no connection

INV - inverting terminal

NINV - non inverting terminal

V_{ref} - reference voltage

V^- - -ve voltage

NC - no connect

V_Z - zener voltage


V_{out} - output voltage

V_C - internal voltages

V^+ - +ve voltage

13 - frequency variations

14 - No connection

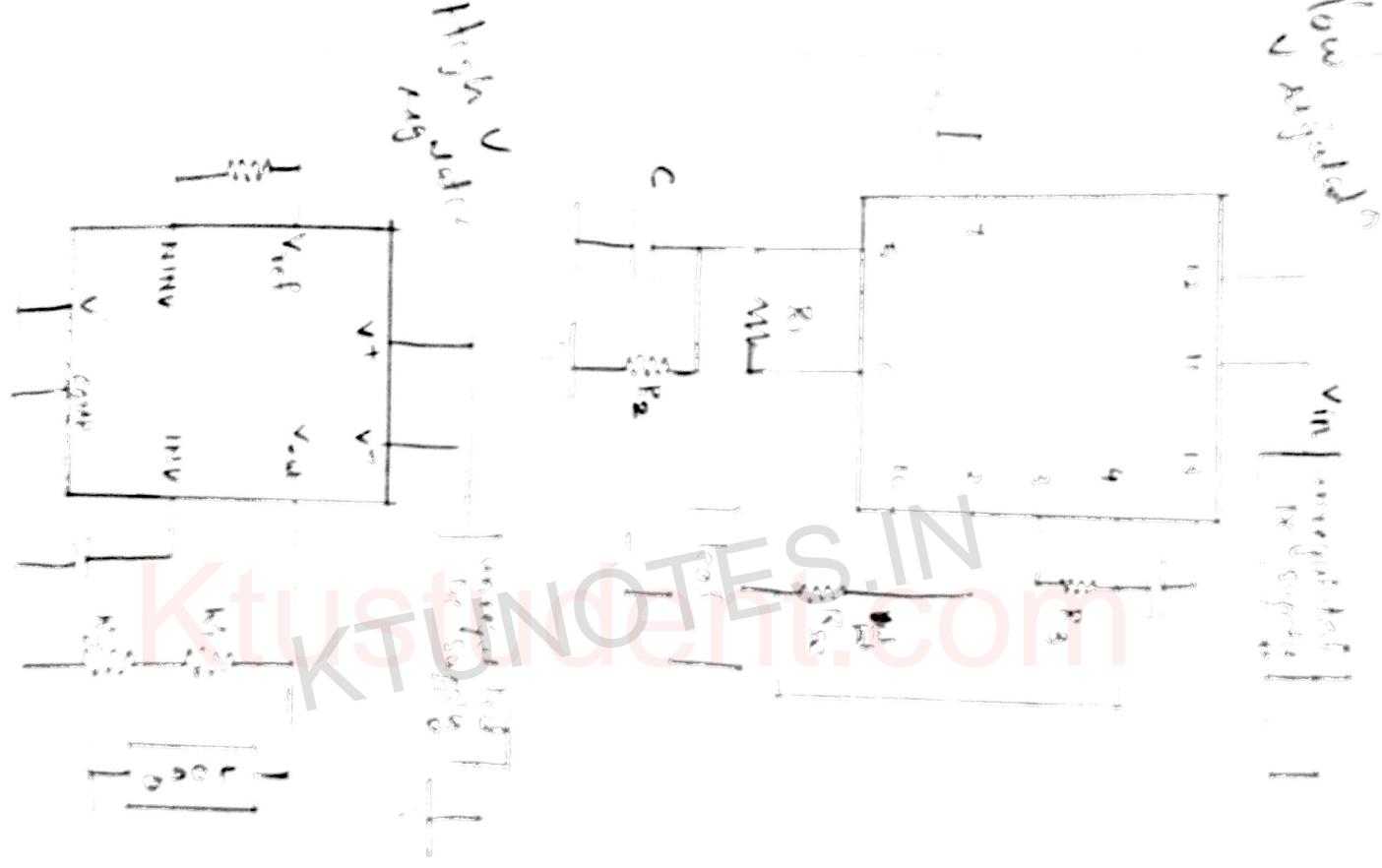

100
100

linear
regulators.

SWITCH MODE POWER SUPPLY

Linear regulator - power consumption is high
SMPS - " low

SMPS - transistor is either in saturation region

or in cutoff region.

∴ power consumptn low, efficiency high

on state : saturated region



off state : cutoff region

transistor
task



→ Step-down version

→ step up "

→ Polarity inverting "

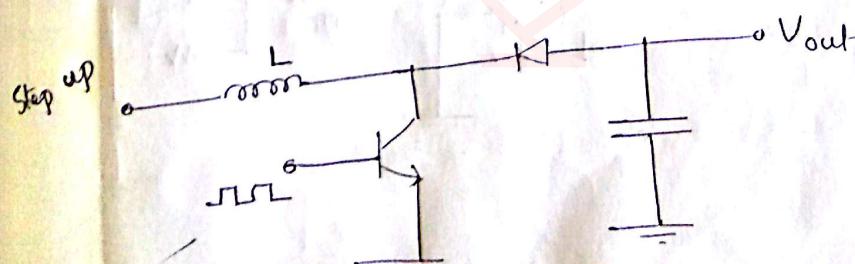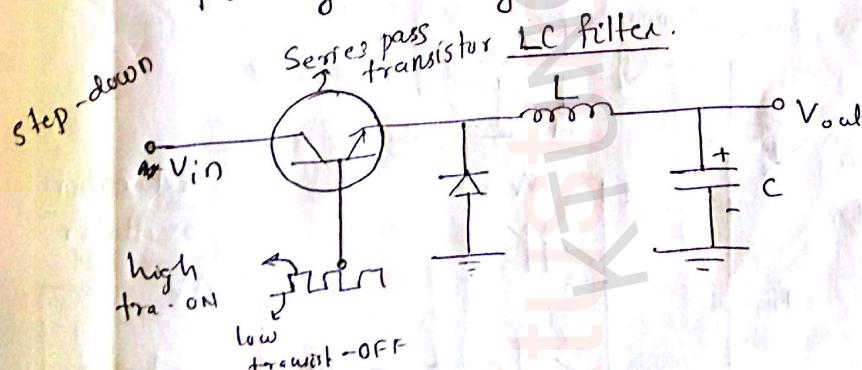

Polarity inverting

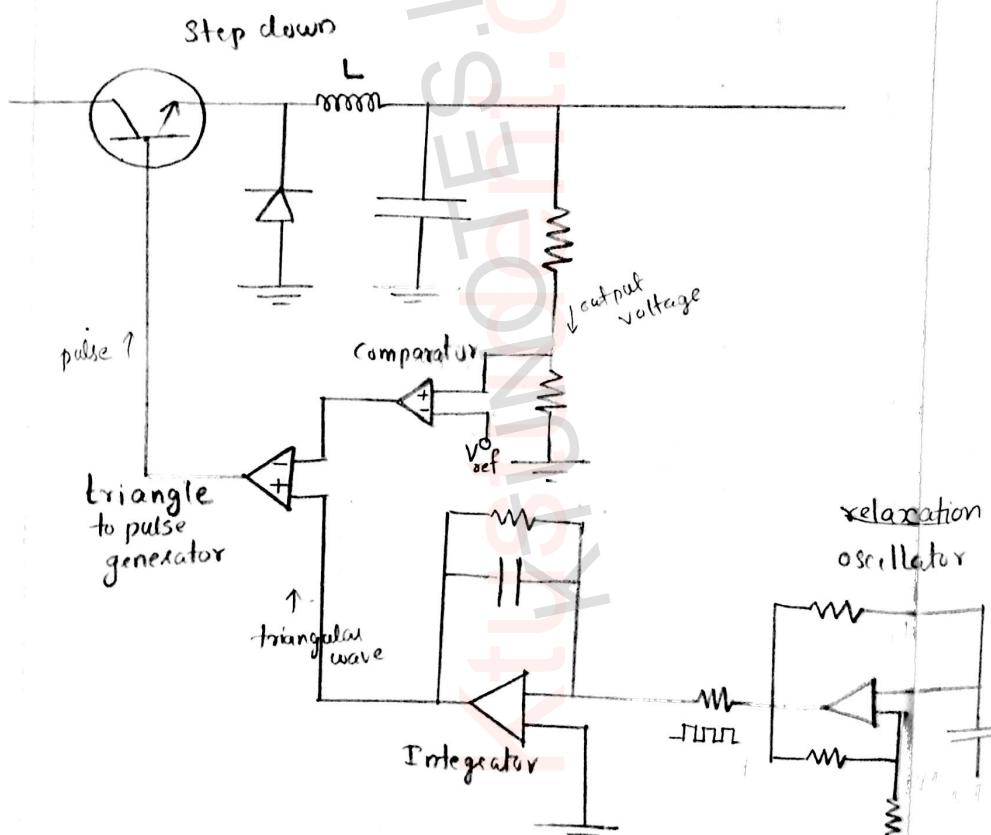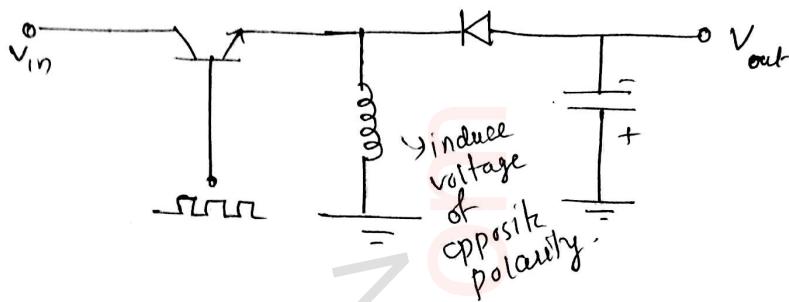

Field Effect Transistors (FET)

Conduction is due to electric field


- 1) Source
- 2) Drain
- 3) Gate


FET is a uni polar device.


FET is stable at higher temp.

BJT \rightarrow current controlled device

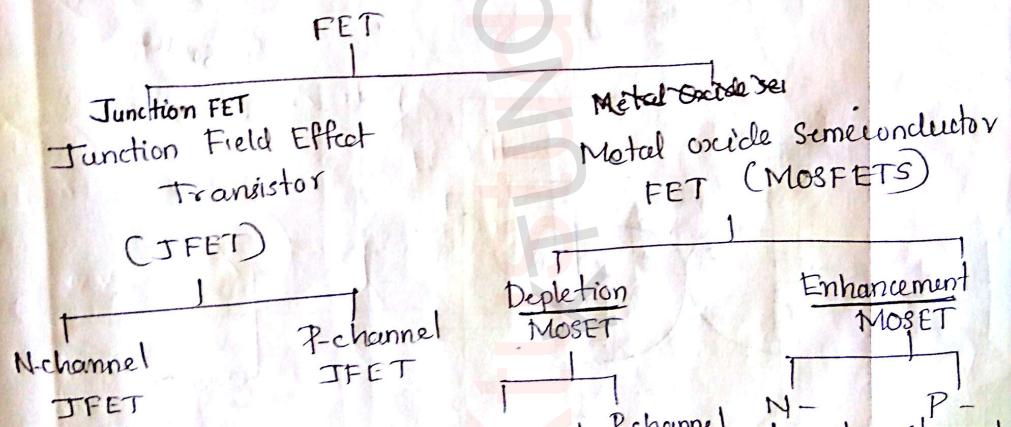FET \rightarrow voltage controlled device



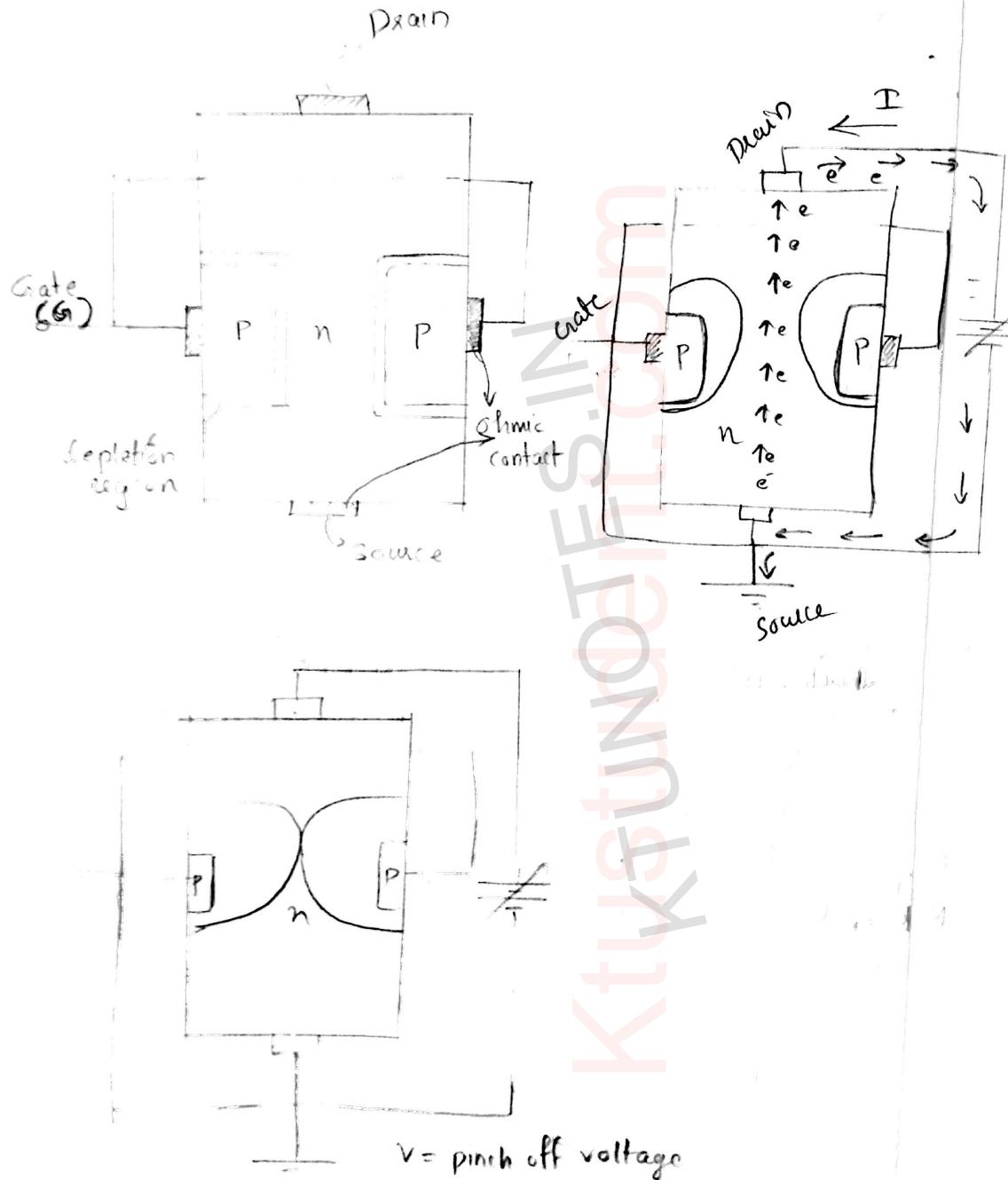

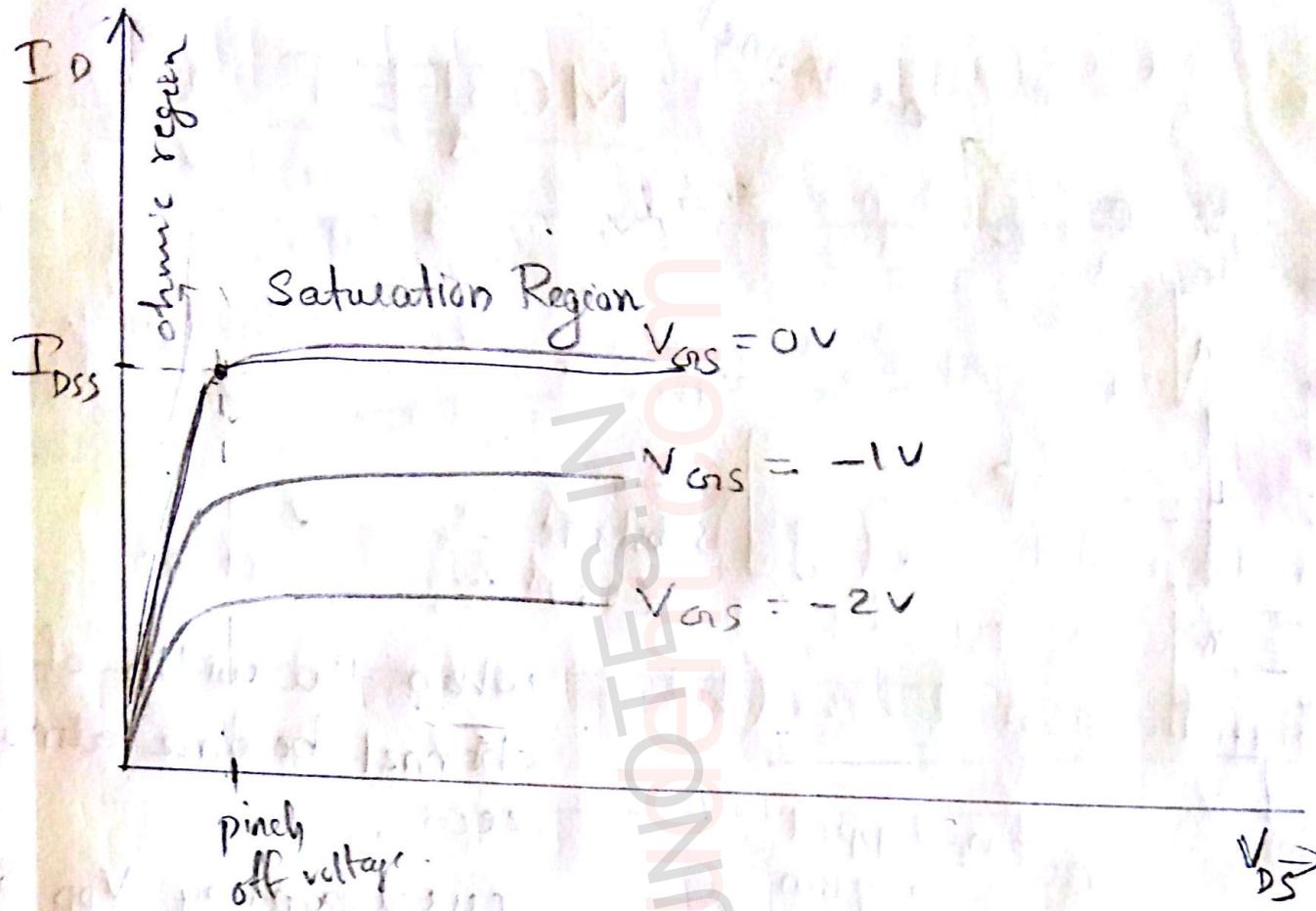

$$I_D = I_{DSS} \left(1 - \frac{|V_{GS}|}{|V_P|} \right)^2$$

$$I_D = I_{DSS} \left(1 - \frac{|V_{GS}|}{|V_P|} \right)^2$$


$$V_{GS} = V_P$$

$$I_D = 0$$

$$V_{GS} = 0$$

$$I_D = I_{DSS}$$

MOSFET

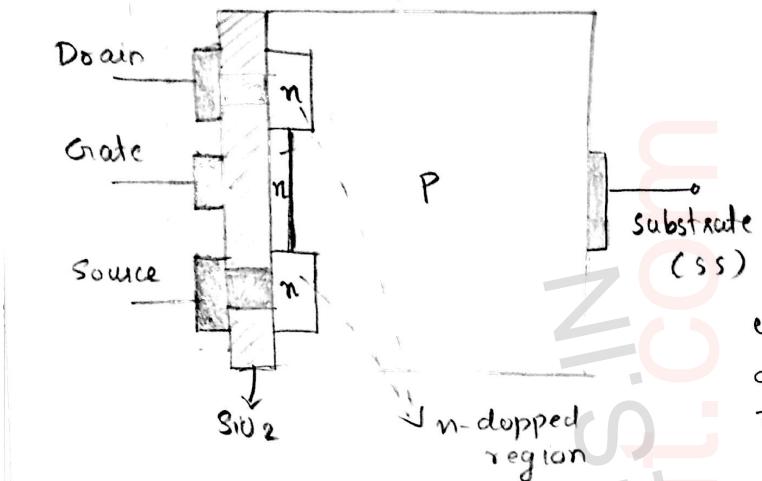



when the width of channel become almost zero,
corresponding V_{DD} is called

pinch-off voltage (V_p)

At that time; the drain current is called saturation drain current

V_{DD} (I_{DSS})

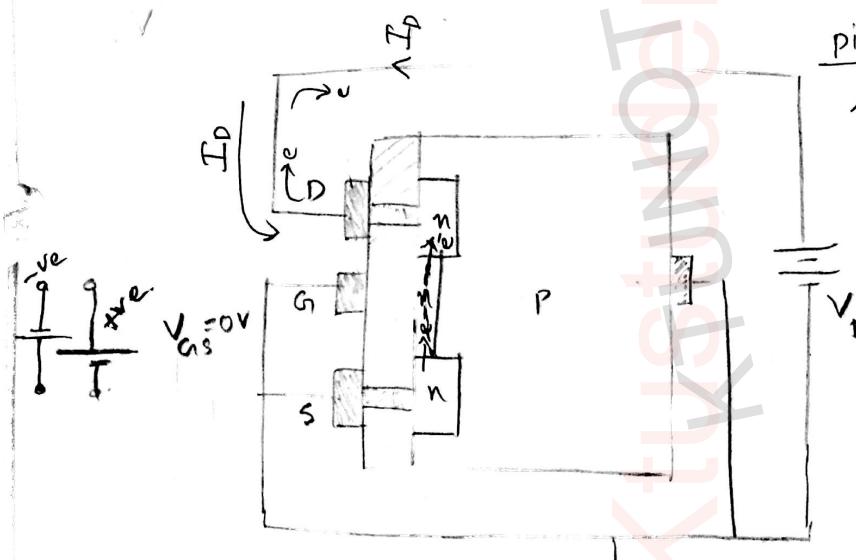


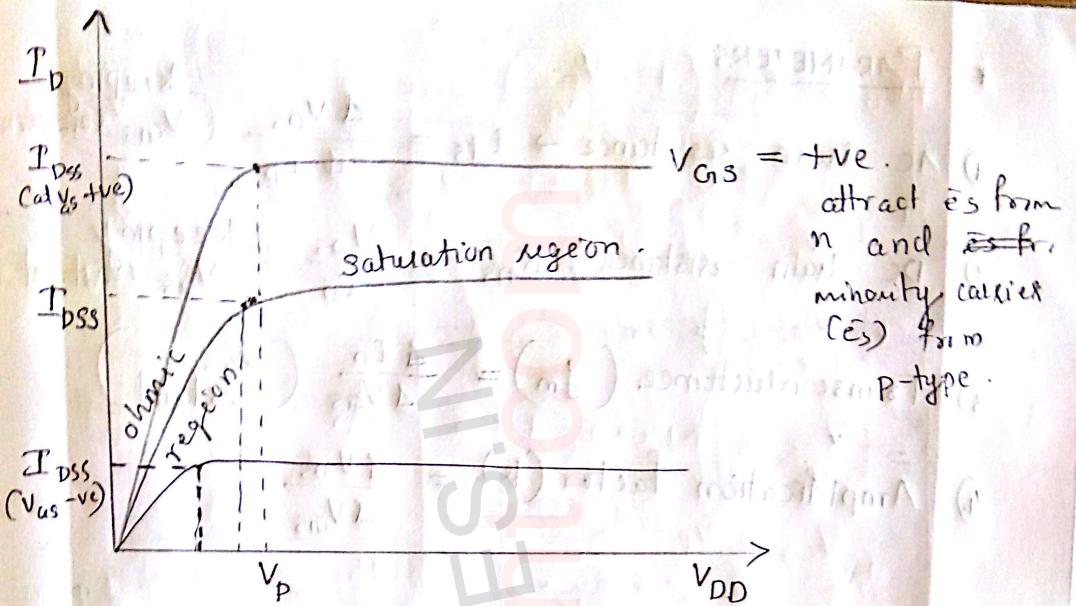

$V_{GS} = +ve.$
 attract $\bar{e}s$ from
 n and ~~from~~
 minority carrier
 $(\bar{e}s)$ from
 p-type.

$V_{GS} = -ve$
 it pushes the electrons to p-region and majority
 carriers in p-region (holes) and thus $\bar{e}s$
 combine. $\therefore \bar{e}s \downarrow$ es \therefore drain current \downarrow
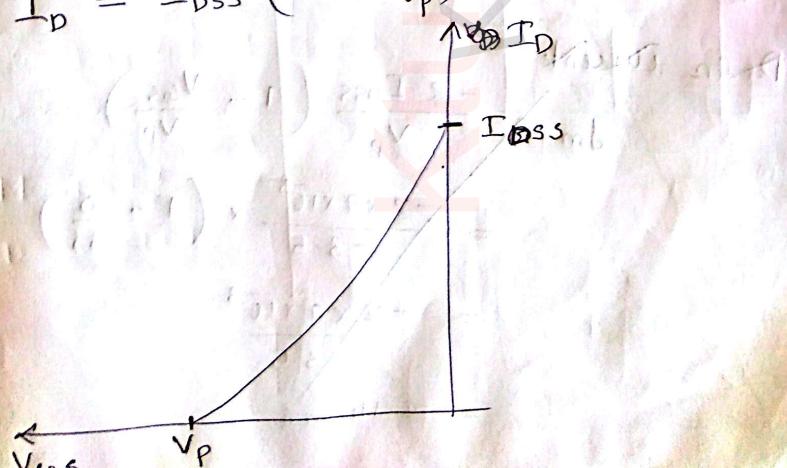
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$



* PARAMETERS

- 1) AC drain resistance $\rightarrow R_{ds} = \frac{\Delta V_{DS}}{\Delta I_D}$ (keeping V_{GS} constant)
- 2) DC drain resistance, $R_{DS} = \frac{V_{DS}}{I_D}$ (keeping V_{GS} constant)
- 3) Transconductance (g_m) = $\frac{\Delta I_D}{\Delta V_{GS}}$ (V_{DS} constant)
- 4) Amplification factor (μ) = $\frac{\Delta V_{DS}}{\Delta V_{GS}}$

ans

'Drain' Transconductance

$\frac{d I_D}{d V_{GS}}$

$$g_m = -\frac{2 I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$\mu = g_m \times R_{ds}$$

Given $I_{DSS} = 9 \text{ mA}$ and $V_P = -3.5 \text{ V}$. Determine I_D
when $V_{GS} = 0 \text{ V}$ and $V_{DS} = -2 \text{ V}$

Drain current

$$\begin{aligned} g_m &= -\frac{2 I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right) \\ &= -\frac{2 \times 9 \times 10^{-3}}{-3.5} \times \left(1 - \frac{0}{-3.5}\right) \\ &= -\frac{2 \times 9 \times 10^{-3}}{-3.5} \\ &= 5.14 \text{ mA} \end{aligned}$$

$$g_m(v_{as}) = \frac{2 \times 9 \times 10^{-3}}{-3.5} \left(1 - \frac{-2}{-3.5}\right)$$

$$= 1.$$

- 2) A JFET has pinch off voltage as -1.5 V
 $I_{DSS} = 10\text{ mA}$ and $I_D = 2.5\text{ mA}$. Determine the transconductance.

ans 1)

$$I_D = I_{DSS} \left(1 - \frac{v_{as}}{V_p}\right)$$

$$(v_{as} = 0\text{ V})$$

$$= 9 \times 10^{-3} \times 1 = 9\text{ mA}$$

$$I_D = I_{DSS} \left(1 - \frac{\frac{-1.5 + 2}{-3.5}}{1}\right)$$

$$(v_{as} = -2\text{ V})$$

$$= 9 \times 10^{-3} \left(1 - \frac{2}{3.5}\right)^2$$

$$= \underline{\underline{1.65\text{ mA}}}$$

I_D

2)

$$V_p = -1.5\text{ V}$$

$$I_{DSS} = 10\text{ mA}$$

$$I_D = 2.5\text{ mA}$$

$$\cancel{g_m} =$$

$$I_D = I_{DSS} \left(1 - \frac{v_{as}}{V_p}\right)^2$$

$$1 - \frac{v_{as}}{V_p} = \frac{I_D}{I_{DSS}} = \frac{(2.5)}{10} = (0.25)^2 = 0.0625$$

$$\frac{v_{as}}{V_p} = 1 + 0.0625 = 1.0625$$

$$v_{as} = V_p \times 1.0625 = -1.5 \times 1.0625 = -1.625$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

ans
 $V_{GS} = 2.25$

$$\left(1 - \frac{V_{GS}}{V_P}\right)^2 = \frac{I_D}{I_{DSS}} = \frac{2.5}{10} = 0.25$$


$$g_S = 2.2 \text{ mA}$$

$$1 - \frac{V_{GS}}{V_P} = \sqrt{0.25} = 0.5$$

$$\frac{V_{GS}}{V_P} = 1 - 0.5 = 0.5$$

$$V_{GS} = V_P \times 0.5 \\ = -1.5 \times 0.5 = \underline{\underline{0.75}}$$


Enhancement - MOSFET

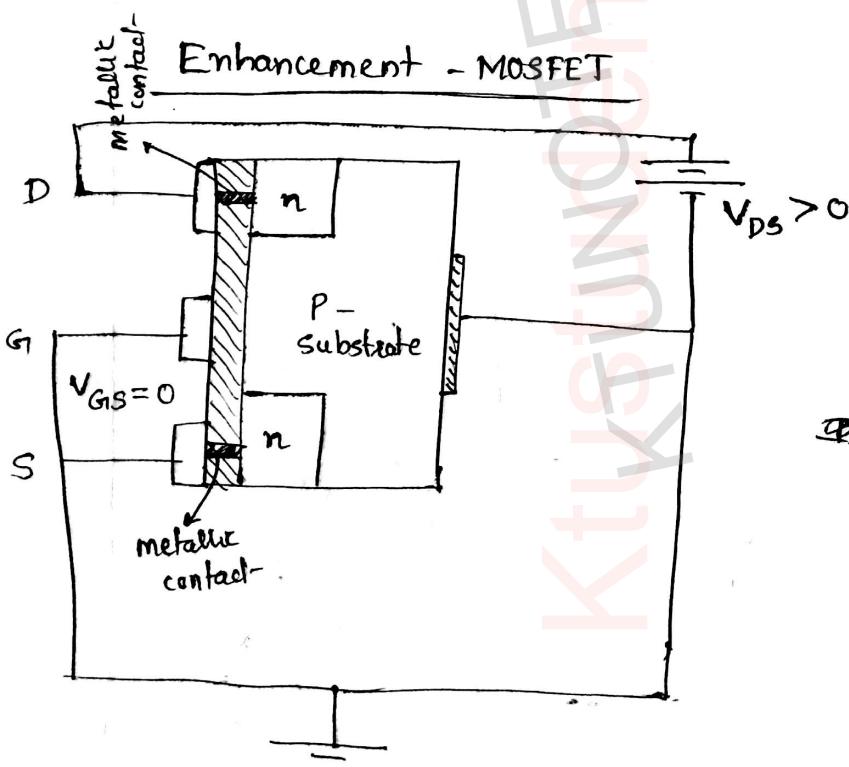

2.25

2.2 mA

$$I_D = 0$$

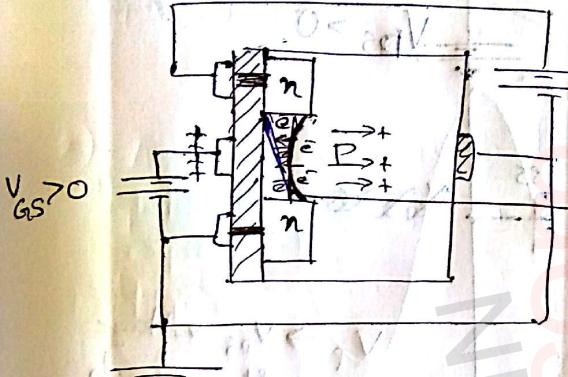

$$V_{DS} = 5V$$

(fixed)

channel formed
 V_{GS} at which channel is
formed, it is called
threshold voltage (V_T)

1) when $V_{GS} > V_T$, channel width increases

when V_{GS} increases, $I_D \uparrow$.

channel width is constant

2) V_{GS} constant

and $V_{DS} > 0$ increases. \therefore channel width is
increases $I_D \uparrow$ in the channel


when $V_{DS} > 0$ increases \therefore channel width \downarrow

decreases, \therefore channel width \downarrow


$I_D \downarrow$ upto a constant value called pinch-off


current I_{DSS} . At that time V_{DS} is called

pinch-off voltage.

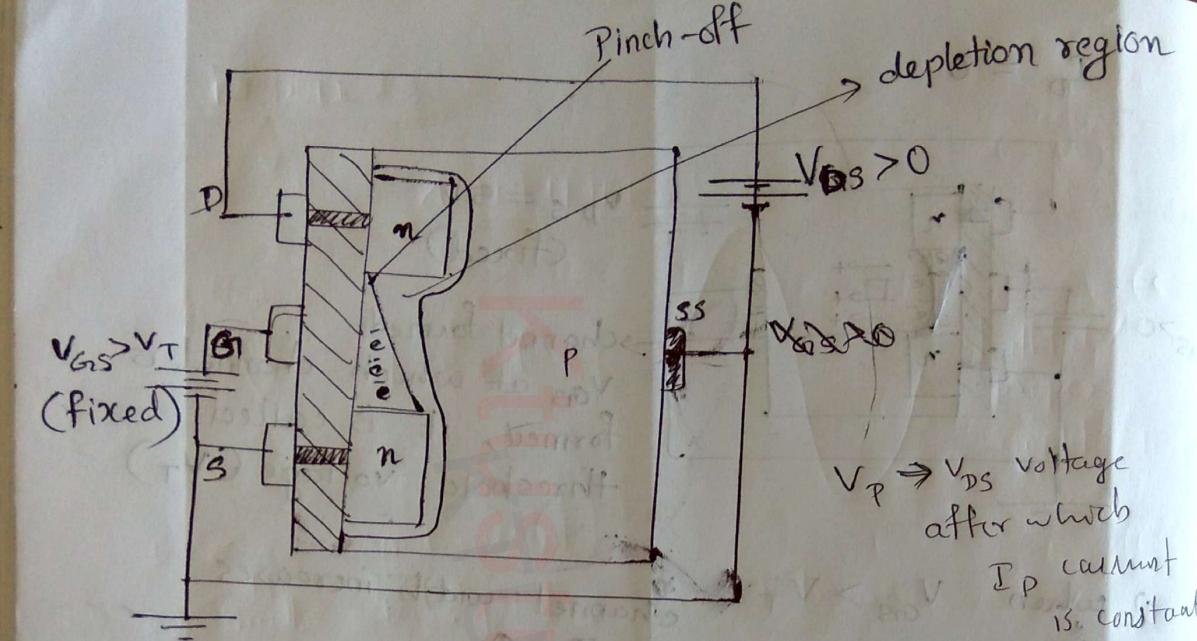

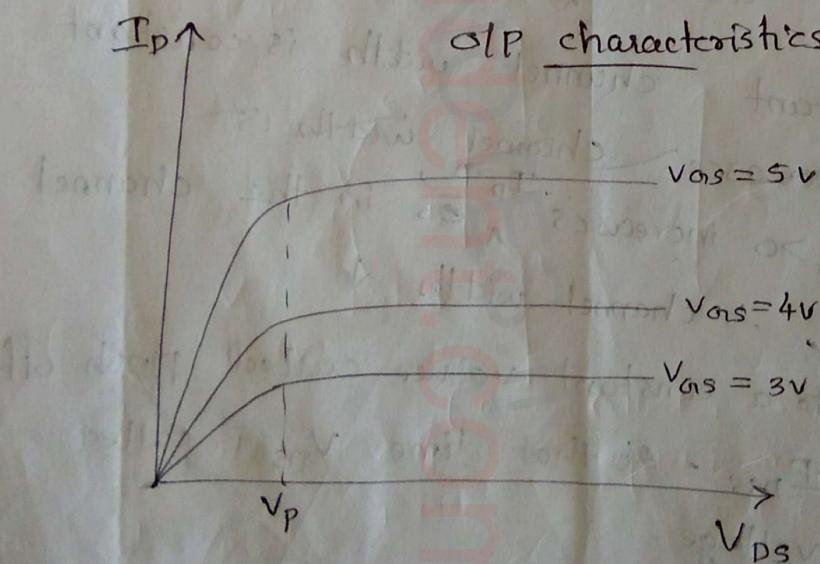$V_P \Rightarrow V_{DS}$ voltage after which I_D current is constant



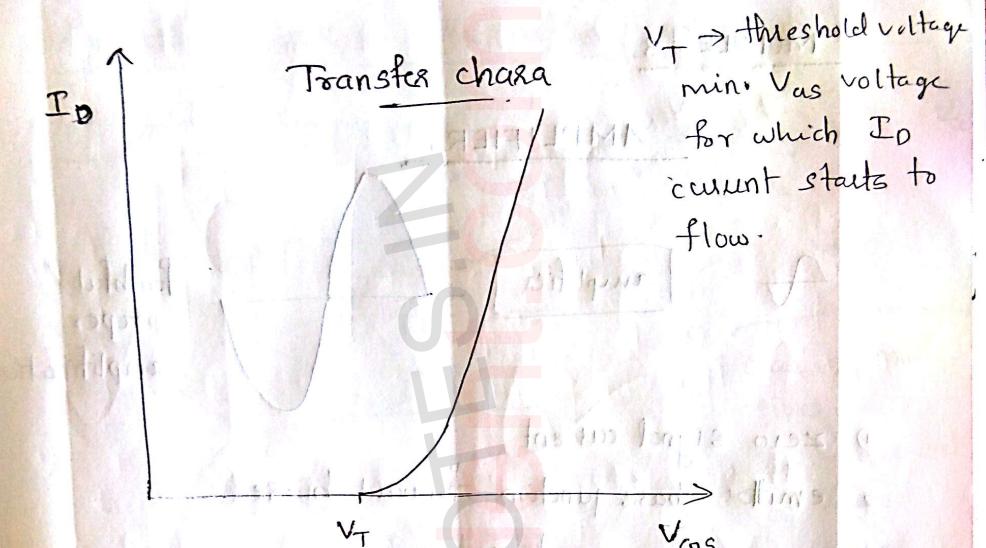

5
must
constant

$$I_D = k(V_{GS} - V_T)^2$$

$$k = \frac{I_{D(\text{on})}}{(V_{GS(\text{on})} - V_T)^2}$$

$$V_{GD} = V_{DS} - V_{GS}$$

In Enhancement MOSFET
Initially no channel. Enhanced \rightarrow creating
the channel. But in depletion MOSFET there
the channel is already present.